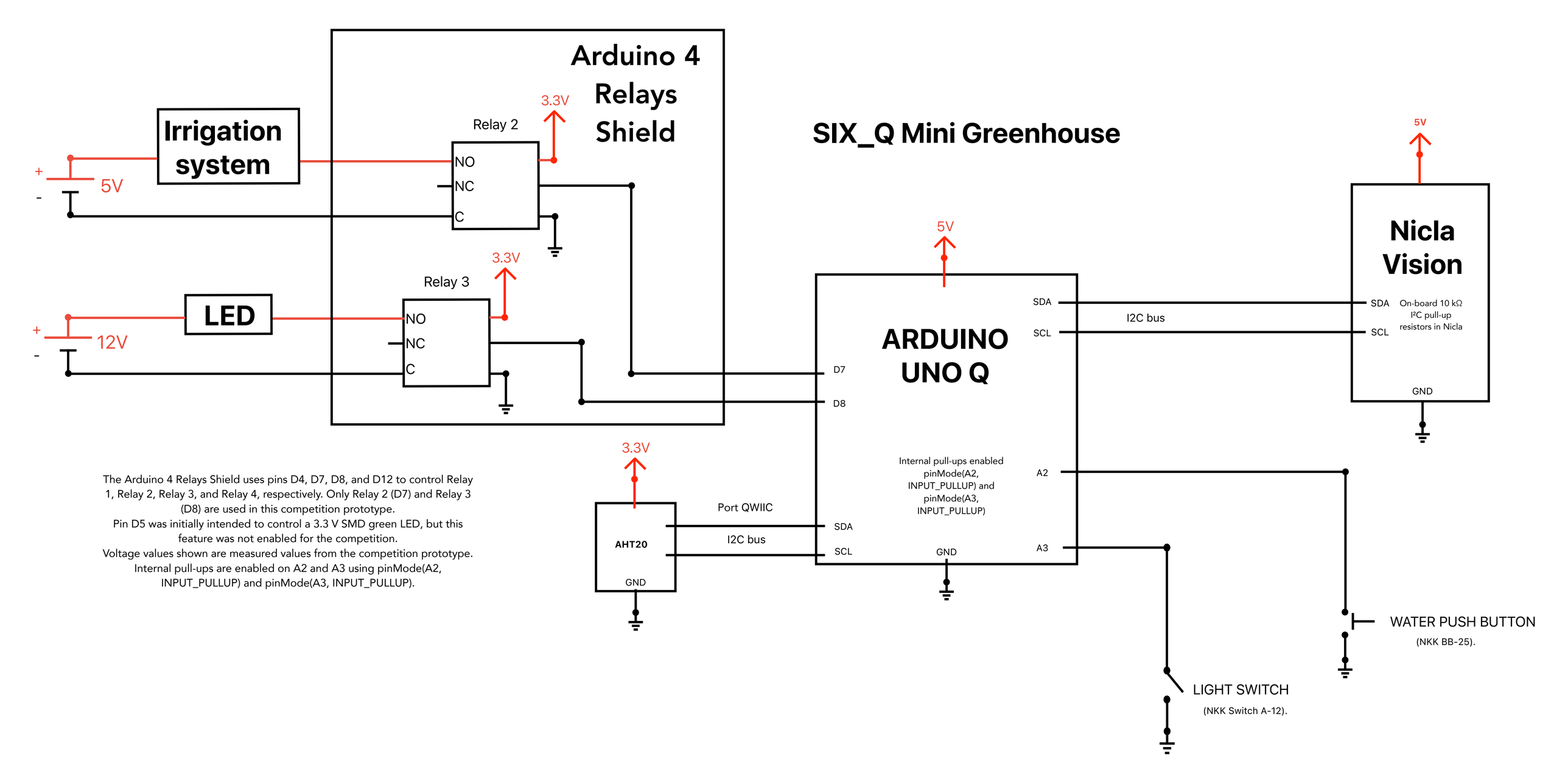


The Arduino 4 Relays Shield uses pins D4, D7, D8, and D12 to control Relay 1, Relay 2, Relay 3, and Relay 4, respectively. Only Relay 2 (D7) and Relay 3 (D8) are used in this competition prototype.
Pin D5 was initially intended to control a 3.3 V SMD green LED, but this feature was not enabled for the competition.
Voltage values shown are measured values from the competition prototype.
Internal pull-ups are enabled on A2 and A3 using pinMode(A2, INPUT_PULLUP) and pinMode(A3, INPUT_PULLUP).